

## Numerical Problems

**14.1 A current of 3mA is flowing through a wire for 1 minute. What is the charge flowing through the wire?**

**Answer**

$$\text{Current, } I = 3 \text{ mA}$$

$$= 3 \times 10^{-3} \text{ A}$$

$$\text{Time, } t = 1 \text{ min}$$

$$= 60 \text{ sec.}$$

$$\text{Charge, } Q = ?$$

As we know that,

$$I = Q/t, \text{ or } Q = It$$

Putting the values, we get,

$$Q = 3 \times 10^{-3} \times 60$$

$$\boxed{Q = 180 \times 10^{-3} \text{ C}}$$

**14.2 At  $100,000 \Omega$  how much current flows through your body if you touch the terminals of a 12 V battery? If your skin is wet, so that your resistance is only  $1000\Omega$ , how much current would you receive from the same battery?**

**Answer**

$$\text{Resistance, } R = 10000 \Omega$$

$$= 10^5 \Omega$$

$$\text{Current, } I = ?$$

Voltage,  $v = 12 \text{ V}$

Resistance of wet skin,  $R' = 1000 \Omega$

Current flowing through we skin,  $I' = ?$

**i) For dry skin**

applying ohm's law, we have:

$$V = IR$$

$$\text{Or, } I = V/R$$

Putting the values, we get,

$$I = \frac{12}{10^5}$$

$$\boxed{I = 1.2 \times 10^{-4} \text{ A}}$$

**ii) For wet skin**

Again, applying ohm's law, we get,

$$V' = I' R', \text{ or } I' = V/R'$$

Putting the values, we get,

$$I = 12/1000$$

$$\text{or } \boxed{I' = 1.2 \times 10^{-2} \text{ A}}$$

**14.3 The resistance of a conductor wire is  $10 \text{ M}\Omega$ . If a potential difference of  $100 \text{ V}$  applied across its ends, then find the value of current passing through it in mA.**

**Answer**

Resistance,  $R = 10 \text{ M}\Omega$

$$= 10 \times 10^6 \Omega$$

Voltage,  $V = 100 \text{ V}$

$$\text{Current (mA)} = I \text{ (mA)} = ?$$

Applying ohm's law, we get:

$$V = IR$$

$$I = V/R$$

$$\Rightarrow I = 100/10^7$$

$$I = 10^{-5} \text{ A}$$

As we know that,  $1 \text{ A} = 10^3 \text{ mA}$ ,

$$I = 0.01 \text{ mA}$$

**14.4, By applying a potential difference of 10 V across a conductor a current of 1.5 A passes through it. How much energy would be obtained from the current in 2 minutes?**

**Answer**

$$\text{Voltage, } V = 10 \text{ V}$$

$$\text{Current, } I = 1.5 \text{ A}$$

$$\text{Energy obtained} = ?$$

$$\text{Time, } t = 2 \text{ min}$$

$$= 120 \text{ sec.}$$

As we know according to Joule's law, we get:

$$\text{Energy} = VIt$$

Putting the values, we get,

$$\text{Energy} = 10 \times 1.5 \times 120$$

$$\text{Energy obtained} = 1800 \text{ J}$$

**14.5** Two resistance of  $2\text{k}\Omega$  and  $8\text{k}\Omega$  are joined in series, if a  $10\text{ V}$  battery is connected across the ends of this combination, find the following quantities:

- The equivalent resistance of the parallel combination.
- Current passing through each of the resistance.
- Potential difference across each of the resistance.

**Answer**

First resistance,  $R = 2\text{k}\Omega$

$$= 2000\Omega$$

Second resistance,  $R_2 = 8\text{k}\Omega$

$$= 8000\Omega,$$

Voltage supplied,  $V = 12\text{ V}$

Equivalent resistance,  $R_{\text{eq}} = ?$

As the resistance are joined in series,

$$I_1 = I_2 = I = ?$$

Voltage across  $R_1$ ,  $V_1 = ?$

Voltage across  $R_2$ ,  $V_2 = ?$

We know that:

$$R_{\text{eq}} = R_1 + R_2$$

$$\Rightarrow = 2\text{k}\Omega + 8\text{k}\Omega$$

Also, for current; applying ohm's law;

$$V = IR_{\text{eq}}$$

$$I = V/R_{\text{eq}}$$

$$= 12/10,000$$

$$I = 0.001\text{ A}$$

$$I = 1\text{mA}$$

$$I = I_1 = I_2, \text{ So } \boxed{I_2 = I_2 = 1\text{ mA}}$$

For voltage, again applying ohm's law,

1) For resistance  $R_1$ ,

$$\begin{aligned} \Rightarrow V_1 &= IR_1, \\ &= 0.001 \times 2000 \end{aligned}$$

$$\boxed{V_1 = 2\text{V}}$$

2) for resistance  $R_2$ ,

$$\begin{aligned} \Rightarrow V_2 &= IR_2, \\ &= 0.001 \times 8000 \end{aligned}$$

$$\boxed{V_2 = 8\text{V}}$$

**14.6** Two resistance of  $6\Omega$  and  $12\Omega$  are connected in parallel. A  $6\text{V}$  battery is connected across its ends, find the values of the following quantities.

- Equivalent resistance of the parallel combination.
- Current passing through each of the resistance.
- Potential difference across each of the resistance.

**Answer**

First resistance,  $R_1 = 6\text{k}\Omega$

$$= 6000\Omega$$

Second resistance,  $R_2 = 12\text{k}\Omega$

$$= 12000\Omega$$

Voltage supplied,  $V = 6\text{V}$

Equivalent resistance,  $R_{eq} = ?$

Current through resistance,  $R_{eq} = ?$

Current through resistance,  $R_1 I_1 = ?$

Current through resistance,  $R_2 I_2 = ?$

As the combination is parallel, so,  $V_1 = V_2 = V = ?$

We know that  $1/R_{eq} = 1/R_1 + 1/R_2$

$$= \frac{1}{6k\Omega} + \frac{1}{12k\Omega}$$

$$= \frac{2k\Omega + 1k\Omega}{12k\Omega}$$

$$\frac{1}{R_{eq}} = \frac{3}{12}k\Omega$$

or

$$\boxed{R_{eq} = 4k\Omega}$$

As For parallel combination, voltage remains the same, So,  $V = V_1 = V_2 = 12$  volts.

Or  $V_1 = V_2 = 12$  volts

For current applying ohm's law;

1) For resistance  $R_1$ :

$$V = I_1 R_1$$

$$I_1 = V/R_1$$

or  $= 6/6000$

$$I_1 = 10^{-3}A$$

or

$$\boxed{I_1 = 1mA}$$

2) For resistance  $R_2$ :

$$V = I_2 R_2$$

$$I_2 = V/R_2$$

or  $= 6/12000$

$$I_2 = 5 \times 10^{-4} \text{ A}$$

or  $I_2 = 0.5 \text{ mA}$

**14.7 An electric bulb is marked with 220Vf 100W. Find the resistance of the filament of the bulb. If the bulb is used 5 hours daily, find the energy in kilowatt-hour consumed by the bulb in one month (30 days).**

**Answer**

$$\text{Voltage, } V = 220 \text{ V}$$

$$\text{Power, } P = 100 \text{ W}$$

$$\text{Resistance, } R = ?$$

$$\text{Time, } t = 5 \times 30$$

$$= 150 \text{ hrs.}$$

$$\text{Energy (kwh)} = ?$$

We know that.

$$P = V^2/R$$

or  $R = V^2/P$

Putting the values, we get:

$$R = (220)^2/100$$

or  $R = 484 \Omega$

Also, we know that

$$\text{Energy (KWh)} = \frac{\text{Watt} \times \text{time (hours)}}{1000}$$

$$= \frac{100 \times 150}{1000}$$

Energy consumed in KWh = 15 KWh

**14.8 An incandescent light bulb with an operating resistance of  $95 \Omega$  is labelled "150 W". Is this bulb designed for use in a 120V circuit or a 220V circuit?**

**Answer**

Resistance,  $R = 95 \Omega$

Power,  $P = 150 \text{ W}$

Voltage,  $V = ?$

We know that:

$$P = V^2/R$$

or  $V^2 = P \times R$

$$V^2 = 150 \times 95$$

$$V = 119.3 \text{ V}$$

$V = 120 \text{ V}$

$\therefore$  (It has been designed for 120 V)

**14.9 A house is installed with:**

a) 10 bulbs of 50 W each of which are used 5 hours daily.

b) 4 fans of 75 W each of which run 10 hours daily.

c) One T.V of 250W which is used for 2 hours daily.

d) One electric iron of 1000 W which is used for 2 hours daily.

If the cost of one unit of electricity is Rs. 4. Find the monthly expenditure of electricity (one month = 30 days)

**Answer.**

$$\text{a) Energy consumed by bulb (KWh)} = \frac{(10 \times 60) \times (5 \times 30) \text{ hours}}{1000}$$

$$= \frac{600 \text{ W} \times 150 \text{ hrs}}{1000}$$

$$= 90 \text{ KWh}$$

$$\text{b) Energy consumed by fans (KWh)} = \frac{(4 \times 75) \times (10 \times 30) \text{ hours}}{1000}$$

$$= \frac{300 \text{ W} \times 300 \text{ hrs}}{1000}$$

$$= 90 \text{ KWh}$$

$$\text{c) Energy consumed by T.V (KWh)} = \frac{(1 \times 250) \times (2 \times 30) \text{ hours}}{1000}$$

$$= \frac{250 \text{ W} \times 60 \text{ hrs}}{1000}$$

$$= 15 \text{ KWh}$$

$$\text{d) Energy consumed by electric iron (KWh)} = \frac{(1 \times 1000) \times (2 \times 30) \text{ hours}}{1000}$$

$$= \frac{1000 \text{ W} \times 60 \text{ hrs}}{1000}$$

$$= 60 \text{ KWh}$$

$$\text{Total energy consumed} = (90 + 90 + 15 + 60)$$

$$= 255 \text{ KWh}$$

Monthly expenditure of electricity = Total energy consumed x cost per unit.

$$= 255 \times 4$$

$$= \boxed{\text{Rs. 1020/-}}$$

**14.10 A 100 W lamp bulb and a 4kW water heater are connected to a 250 V supply. Calculate (a) the current which flows in each appliance (b) the resistance of each appliance when is use.**

**Answer**

$$\text{Power of bulb, } P_1 = 100 \text{ W}$$

$$\text{Power of water heater, } P_2 = 4 \text{ KW}$$

$$= 4000 \text{ W}$$

$$\text{Voltage, } V = 250 \text{ V}$$

$$\text{Current through bulb, } I_1 = ?$$

$$\text{Current through water heater, } I_2 = ?$$

$$\text{Resistance of bulb, } R_1 = ?$$

$$\text{Resistance of water heater; } R_2 = ?$$

$$1) \text{ For bulb; we have, } P_1 = VI_1,$$

$$= I_1 = P_1/V$$

$$\text{or } I_1 = 100/250$$

$$\boxed{I_1 = 0.4 \text{ A}}$$

$$\text{For resistance, we apply ohm's law}$$

$$= V = I_1 R$$

$$\text{or } R_1 = \frac{V}{I_1}$$

$$R_1 = \frac{250}{0.4}$$

$$\boxed{R_1 = 625 \Omega}$$

$$2) \text{ For water heater; we have;}$$

$$P_2 = VI_2$$

$$\text{Or } I_2 = P_2/V$$

$$= 4000/250$$

$$\boxed{I_2 = 16 \text{ A}}$$

And,

$$V = I_2 R_2$$

$$R_2 = V/I_2$$

$$= 250/16$$

$$\boxed{R_2 = 15.6 \Omega}$$

**14.11** A resistor of resistance  $5.6\Omega$  is connected across a battery of  $3.0\text{ V}$  by means of wire of negligible resistance. A current of  $0.5\text{ A}$  passes through the resistor. Calculate

- power dissipated in the resistor
- total power produced by the battery
- Give the reason of difference between these two quantities

**Answer**

Resistance of resistor,  $R = 5.6 \Omega$

Voltage across battery,  $V = 3\text{ V}$

Current through resistor,  $I = 0.5\text{ A}$

Power dissipated in resistor,  $P = ?$

Total power produced by battery,  $P' = ?$

1) For Resistor R:

We know that,  $P = I^2 R$

$$= (0.5)^2 \times 5.6$$

$$\therefore \boxed{P = 1.4\text{ W}}$$

2) For battery:

As the internal resistance of battery is not known so,

$$V = IR'$$

$$R' = V/I$$

Or  $R' = 3/0.5$

$$R' = 6\Omega$$

It means that battery has resistance =  $R' - R = 6 - 5.6$

$$= 0.4 \Omega$$

So, power produced by the battery;

$$P' = I^2 R'$$

$$= (0.5)^2 \times 6$$

$$\boxed{P' = 1.5 \text{ W}}$$

