

## Numerical Problems

**15.1** A transformer is needed to convert a mains 240 V supply into a 12 V supply. If there are 2000 turns on the primary coil, then find the number of turns on the secondary coil.

**Answer**

Input voltage,  $V_p = 240 \text{ V}$

Output voltage,  $V_s = 12 \text{ V}$

Turns on primary coil,  $N_p = 2000$

Turns on secondary coil,  $N_s = ?$

By the formula of turn ratio in transformer,

We have:

$$\frac{V_s}{V_p} = \frac{N_s}{N_p}$$

or 
$$N_s = \frac{V_s}{V_p} \times N_p$$

Putting the values, we get:

$$N_s = \frac{12}{240} \times 2000$$

$$\boxed{N_s = 100 \text{ turns}}$$

**15.2** A step-up transformer has a turn ratio of 1: 100. An alternating supply of 20 V is connected across the primary coil. What is the secondary voltage?

**Answer**

{ As the turn ratio is given, i. e.  $N_p : N_s$   
{ in step – up transformer, or 1: 100

It means, that:  $\frac{N_s}{N_p} = \frac{100}{1}$

Also, input voltage,  $V_p = 20 \text{ V}$

Output voltage,  $V_s = ?$

Applying the formula:

$$\frac{V_s}{V_p} = \frac{N_s}{N_p}$$

Putting the values, we get:

$$\frac{V_s}{20} = \frac{100}{1}$$

$$V_s = 20 \times 100$$

$$V_s = 2000 \text{ volts}$$

**15.3 A step-down transformer has a turns ratio of 1: 100. An A.C voltage of amplitude 170 V is applied to the primary. If the current in the primary is 1.0 mA, what is the current in the secondary?**

**Answer**

As a step-down transformer is given; So:

$$N_p : N_s$$

It means that, 100 : 1

Therefore,  $\frac{N_s}{N_p} = \frac{1}{100}$

Input A.C voltage,  $V_p = 170 \text{ V}$

Output A.C voltage,  $V_s = ?$

Input current,  $I_p = 1 \text{ mA}$

$$= 1 \times 10^{-3} \text{ A}$$

Output current:  $I_s = ?$

We know that

$$\frac{V_s}{V_p} = \frac{N_s}{N_p}$$

or 
$$V_s = \frac{N_s}{N_p} \times V_p$$

putting the values, we get:

$$V_s = \frac{1}{100} \times 170$$

or 
$$V_s = 1.7 \text{ V}$$

Now, applying energy conservation formula

$$V_p I_p = V_s I_s$$

$$\Rightarrow I_s = \frac{V_p I_p}{V_s}$$

Putting the values, we get:

$$I_s = \frac{170 \times 10^{-3}}{1.7}$$

or 
$$I_s = 0.1 \text{ A}$$

**15.1 A transformer, designed to convert the voltage from 240 V A.C. mains to 12 V, has 4000 turns on the primary coil. How many turns should be on the secondary coil? If the transformer were 100 % efficient, what current would flow through the primary coil when the current in the secondary coil was 0.4 A?**

**Answer**

Input voltage,  $V_p = 240 \text{ V}$

Output voltage,  $V_s = 12 \text{ V}$

Input current,  $I_p = ?$

Output current,  $I_s = 0.4 \text{ A}$

Turns on primary coil,  $N_p = 4000$

Turns on secondary coil,  $N_s = ?$

We know that

$$\frac{N_s}{N_p} = \frac{V_s}{V_p}$$

$$\Rightarrow N_s = \frac{V_s}{V_p} \times N_p$$

Putting the values, we get:

$$N_s = \frac{12}{240} \times 4000$$

or  $N_s = 200 \text{ turns}$

Applying energy conservation formula

$$V_p I_p = V_s I_s$$

$$\Rightarrow I_p = \frac{V_s I_s}{V_p}$$

Putting the values, we get:

$$I_p = \frac{12 \times 0.4}{240}$$

or  $I_p = 0.02 \text{ A}$

**15.5 A power station generates 500 MW of electrical power which is fed to a transmission line. What current would flow in the transmission line if the input voltage is 250 KV?**

**Answer**

Input power,  $P = 500 \text{ MW}$

$$= 500 \times 10^6 \text{ W}$$

Input current,  $I_p = ?$

Input voltage,  $V_p = 250 \text{ kv}$

$$= 250 \times 10^3 \text{ V}$$

We know that,

$$P = V_p I_p$$

$$\Rightarrow I_p = \frac{P}{V_p}$$


Putting the values, we get:

$$I_p = \frac{500 \times 10^6}{250 \times 10^3}$$

or  $I_p = 200\text{A}$

or  $I_p = 2 \times 10^3\text{A}$

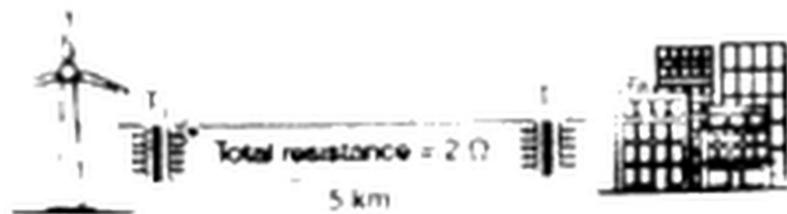15.6 The diagram shows a wind turbine which runs a 150-kW generator with an output voltage of 1000 V. the voltage is increased by transformer  $T_1$  to 10,000 V for transmission to a town 5 km away through power lines with a total resistance of  $2\ \Omega$ . Another transformer,  $T_2$ , at the town reduces the voltage to 250 V. Assume that the transformers are 'ideal'.



When the system is running at full power:

- What is the current in the power line?
- What is the voltage drop and power loss along the power line? Also find the voltage at the input to the town transformer.

**Answer**

Power given to transmission line,  $P = 150\text{ kW}$

$$= 150 \times 10^3\text{ W}$$

Output voltage from transformer,  $T_1$ ,  $V_s = 10000\text{ V}$

Resistance in transmission line,  $R = 2 \Omega$

Current through transmission line,  $I_s = ?$

a) We know that  $P = V_s I_s$

or 
$$I_s = \frac{P}{V_s}$$

Putting the values, we get:

$$I_s = \frac{150 \times 10^3}{10000}$$

$$\boxed{I_s = 15A}$$

b) i): Also, we know that

$$V = IR$$

$$\Rightarrow V = 15 \times 2$$

$$\boxed{V = 30 \text{ volts}}$$

It shows that 30 V voltage will be drop along the power line.

ii) Power along transmission line,  $P' = ?$

We know that,

$$P' = VI$$

$$= 30 \times 15$$

$$\boxed{P' = 450 \text{ W}}$$

It shows that 450 W power will be lost along the transmission line.

iii) Voltage given to transmission line, = 10000 V

Voltage lost along transmission line = 30 V

So,

Voltage at input of  $T_2 = 10000 - 30$

$$= 9970 \text{ V}$$

$$V' = 9970 \text{ V}$$

